

Name- Priyanshi Agarwal


Enrollment No-510519070

From the given STD, we will take inputs.

No of Flip-Flops to be used= $\text{ceil}(\log_2 n)$ where n is no of states

We will understand further algorithm with the help of an example.

Given State Diagram

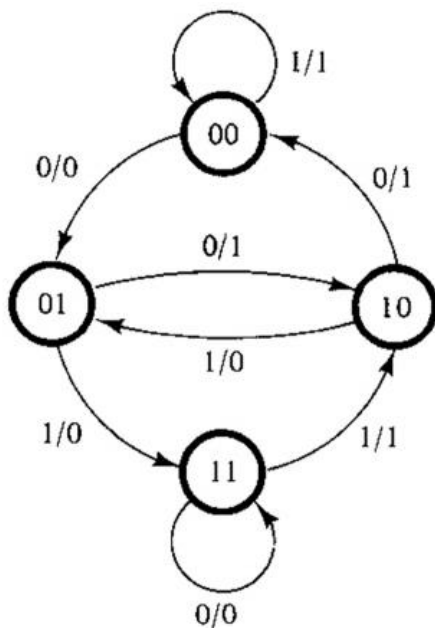

Here $n=4$, So no of flip-flop we will use is $\text{ceil}(\log_2 4)=2$

Let's say we use D-flip flop.

Excitation Table for D-flip-flop :-

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

I (Input)	Y0 (present state)	Y1 (present state)	X0 (next state)	X1 (next state)	Z (Output)	D0	D1
0	0	0	0	1	0	0	1
1	0	0	0	0	1	0	0
0	0	1	1	0	1	1	0
1	0	1	1	1	0	1	1
0	1	1	1	1	0	1	1
1	1	1	1	0	1	1	0
0	1	0	0	1	1	0	1
1	1	0	0	0	1	0	0

Now, We want Equation for Z, D0 and D1. We will use k-map.

$D_0 = y_1$
 $D_1 = \bar{X} y_0 + X \bar{y}_1 + X y_0 y_1$
 $Z = \bar{X} \bar{y}_0 y_1 + X y_0 + y_0 \bar{y}_1 + X y_1$

Now, we will make the circuit using the above Equations.

